

Particle Detectors for the Most Energetic Particles

Rafaela Saraiva ¹ Igor Palha ²

¹Física

Faculdade de Ciencias - Universidade de Lisboa

²Engenharia Física Tecnológica

Instituto Superior Técnico - Universidade de Lisboa

Outline

1 Introduction

2 Equipment

3 Results

4 Conclusions

MARTA - Pierre Auger Observatory

MARTA

Muon
Array with
RPCs for
Tagging
Air Showers



Figure 1: Cherenkov water tanks for cosmic rays detection

RPC - Resistive Plate Chamber

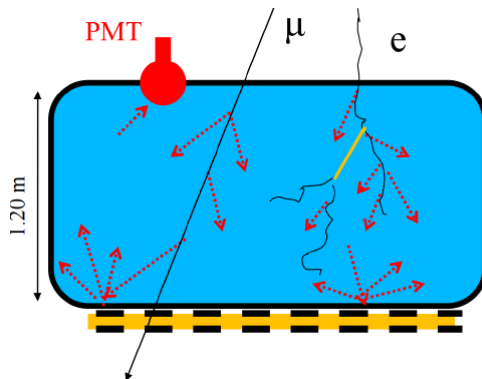


Figure 2: RPC schematic

Outline

1 Introduction

2 Equipment

3 Results

4 Conclusions

Circuit Board



Figure 3: Used Circuit Board

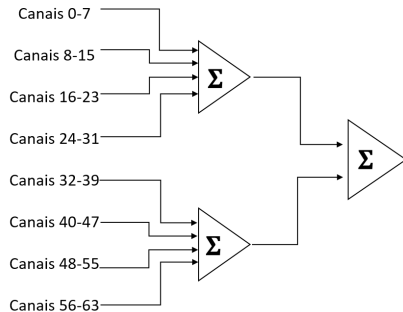


Figure 4: Summation Circuit Schematic

Schematic

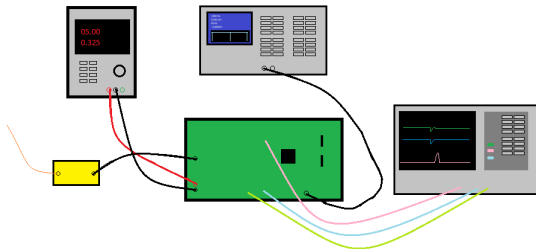


Figure 5: Circuit Setting

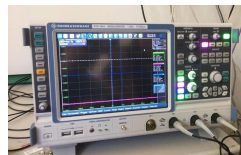


Figure 6: Oscilloscope, Power Supply, Signal Generator and Raspberry Pi

Outline

1 Introduction

2 Equipment

3 Results

4 Conclusions

Signal at the OpAmp

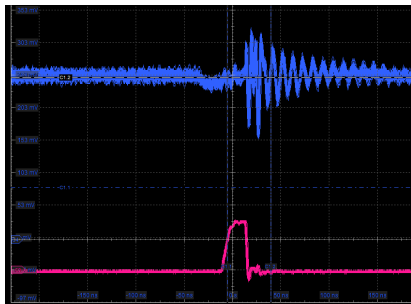


Figure 7: Signal at TP27 with 32 channels on with 64 gain with noise

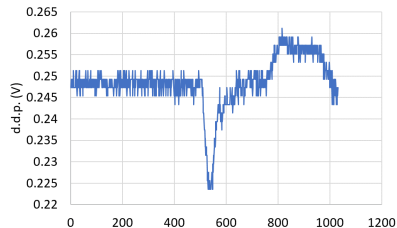


Figure 8: Signal at TP27 with 32 channels on with 128 gain without noise

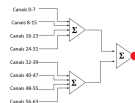


Figure 9: TP27 - Output of the Third

Initial Testing

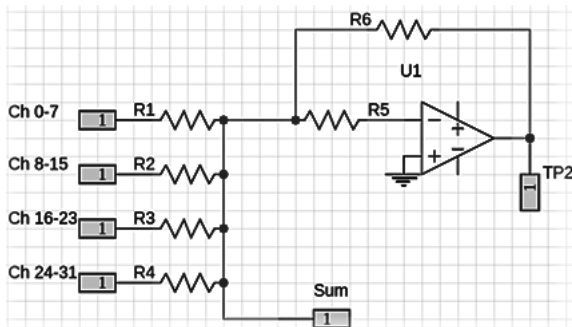


Figure 10: Summation Amplifier Circuit

Voltage Measurements - First OpAmp

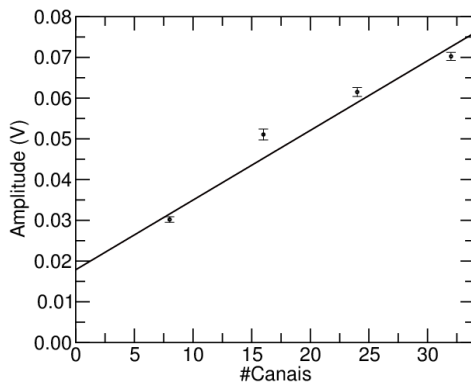


Figure 11: Fit of a linear curve over the voltage of the Summation for a gain of 32

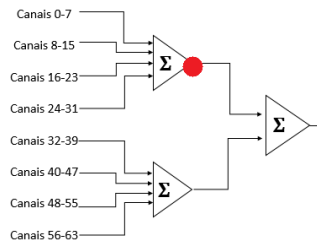


Figure 12: Signal Measured

Voltage Measurements - Second OpAmp

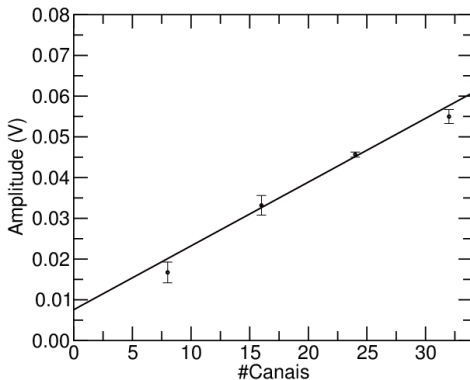


Figure 13: Fit of a linear curve over the voltage of the Summation for a gain of 32

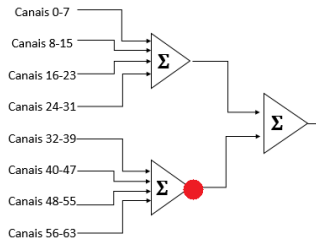


Figure 14: Signal Measured

Voltage Measurements - Third OpAmp

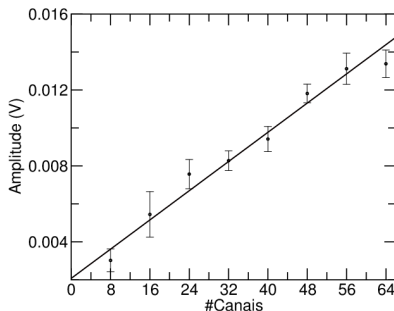


Figure 15: Fit of a linear curve over the voltage of the total Summation for a gain of 32

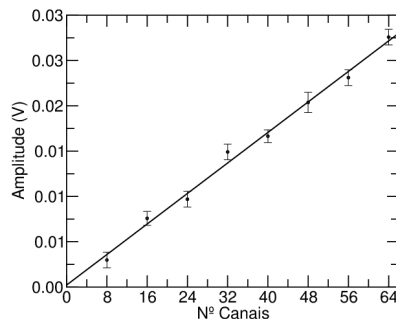


Figure 16: Fit of a linear curve over the voltage of the total Summation for a gain of 64

Voltage Measurements - Third OpAmp

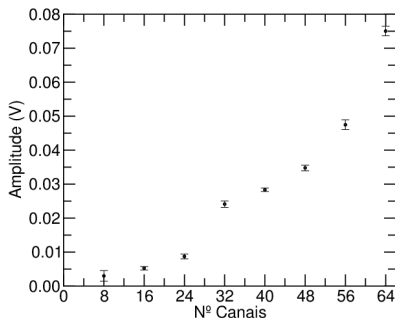


Figure 17: Plot of the voltage of the total Summation for a gain of 128

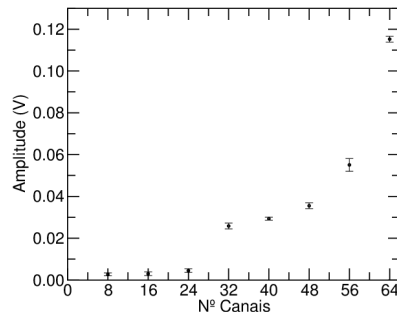


Figure 18: Plot of the voltage of the total Summation for a gain of 256

Charge Measurements

$$q = C.V$$

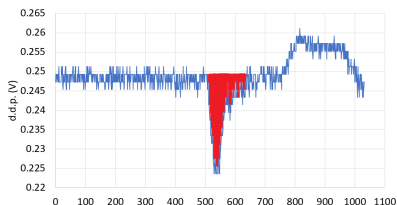


Figure 19: Integral of the Slope Curve to Calculate the Charge

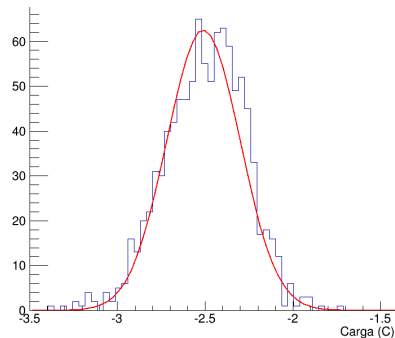


Figure 20: Normal Distribution of the Integrated Charge over 1000 measurements with 48 channels enabled

Charge Measurements

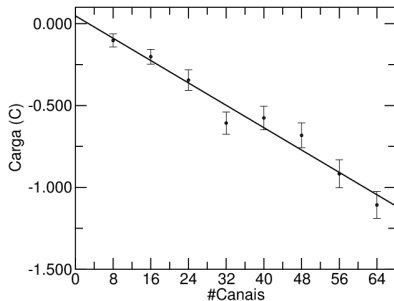


Figure 21: Fit of a linear curve over the integrated Charge of the total Summation for a gain of 32

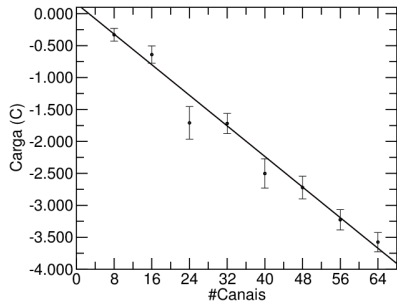


Figure 22: Fit of a linear curve over the integrated Charge of the total Summation for a gain of 64

Charge Measurements

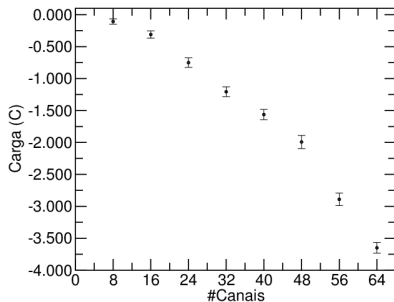


Figure 23: Plot of the integrated Charge of the total Summation for a gain of 128

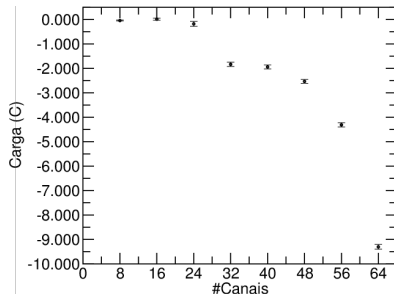


Figure 24: Plot of the integrated Charge of the total Summation for a gain of 256

Outline

1 Introduction

2 Equipment

3 Results

4 Conclusions

Conclusions

The output of the OpAmps didn't behave as previously expected:

- It was expected a symmetry of results on the output signal of the OpAmp 1 and OpAmp 2.
- It was also expected a small gain on the summed signal (Summing Amplifier)

Measuring Problems

There was a significant amount of noise on the measured signal, possibly due to signal reflections, and pickup noise.

Impact on The Project

We helped improving the first part of the circuit board: the group decided to move the summation part to a side board.

The End

Questions ?